

25 Spring ECEN 607: Advanced Analog Circuit Tech
Design Pre-lab Report

Lab4: Op Amp Design - I

Name: Yu-Hao Chen

UIN:435009528

Section:601

Professor: Jose Silva-Martinez

TA: Yoon, Sung J


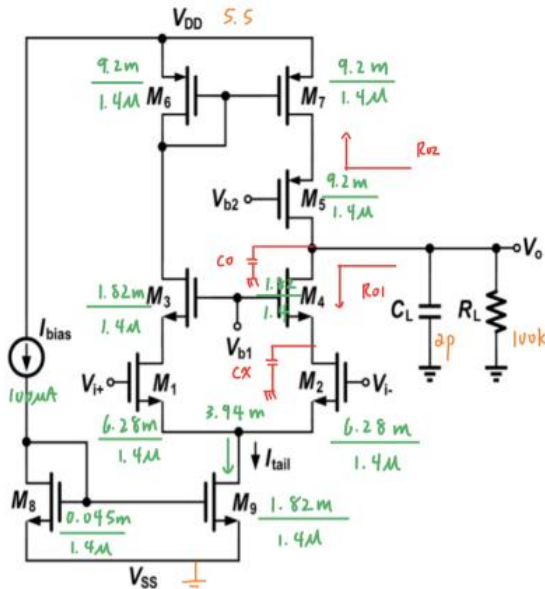


Figure 2-2: Telescopic single stage amplifier

Table 2-2: Design specifications


3163

$V_{DD}-V_{SS}$	5.5 V
A_{v0} ✓	> 70 dB
GBW ✓	> 2 MHz
PM ✓	> 45°
Output Swing @ gain > 40dB ✓	> 0.8 V
C_L	2 pF
R_L	100kΩ
Power Dissipated	< 300 μW
Input referred noise (10 Hz – 2 MHz) ✓	< 30 μVrms

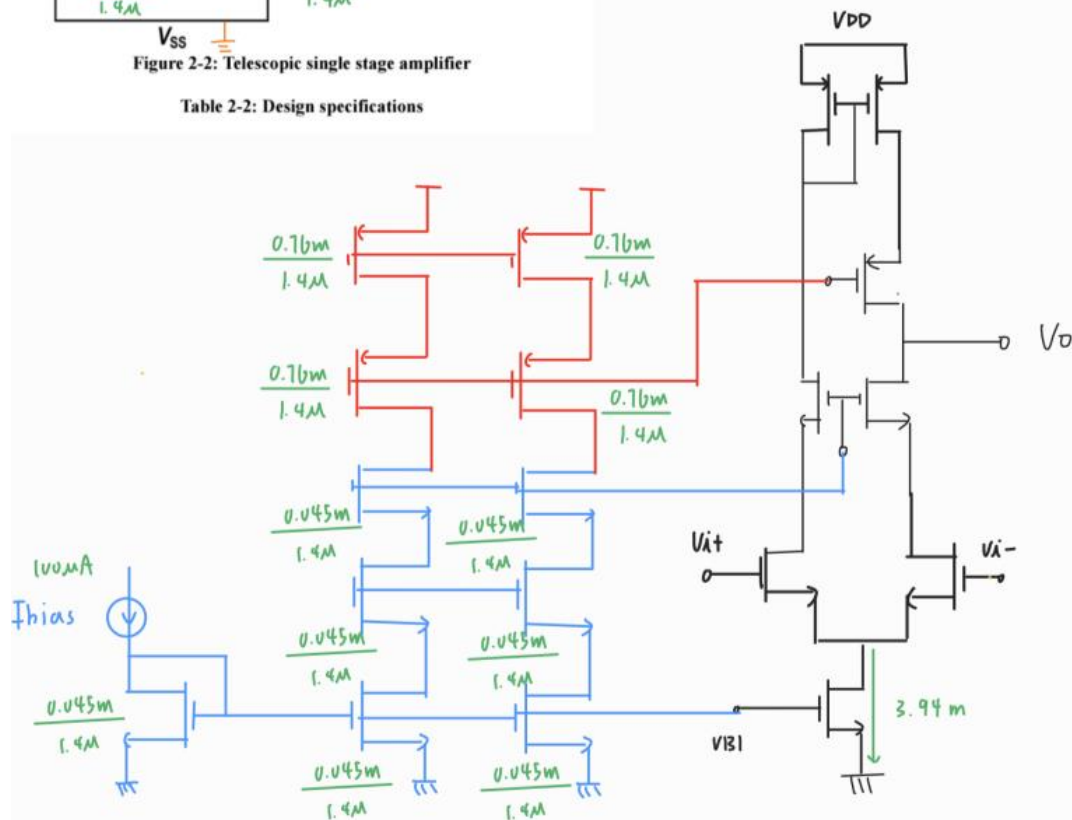

$$Power = I_{total} \times 5.5 \leq 300 \mu W$$

$$I_{total} \leq 5.45 \mu A$$

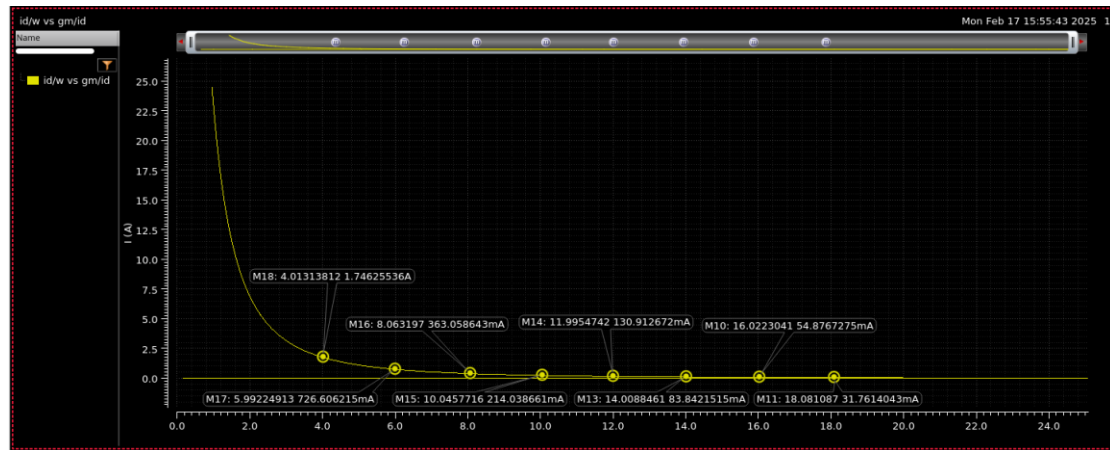

$L=1.4\mu$ pmos G_m/I_D



$L=1.4\mu$ nmos G_m/I_D

$$GBW = \frac{gm_2}{2\pi C_L} \geq 2M \quad gm_2 \geq 25.12 \mu$$

$$w_{p1} = \frac{-1}{C_L (100k \parallel r_{o1} \parallel r_{o2})} \quad \begin{array}{l} r_{o2} \approx gm_5 r_{ds5} r_{ds7} \\ r_{o1} \approx gm_4 r_{ds4} r_{ds2} \end{array} \approx \frac{-1}{2p \times 100k} = 5M$$

$$w_{p2} = \frac{-1}{C_X \left(\frac{1}{gm_4} \parallel r_{ds4} \parallel r_{ds2} \right)} \quad \left| \begin{array}{l} \text{highf } C_L \& C_o \approx \frac{1}{\omega} \end{array} \right. \approx \frac{-1}{100f \times \frac{1}{gm_4}} = \frac{gm_4}{100f}$$

$$A_{vo} = -gm_2 \frac{gm_4 + \frac{1}{r_{ds4}}}{gm_4 + \frac{1}{r_{ds2}} + \frac{1}{r_{ds4}}} \times (r_{o1} \parallel r_{o2} \parallel R_L)$$


$$\approx -gm_2 \times 100k = 3163$$

$$\left. \begin{array}{l} gm_2 (min) = 31.63 m \\ I_{D2} (min) = 1.97 m \end{array} \right\} \frac{gm}{I_D} = 16$$

$$L_2 = 1.4\mu \quad w_2 = 6.28 m$$

output swing :
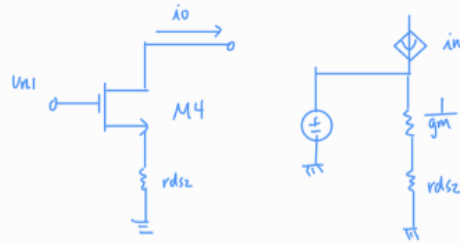
$$\begin{array}{l} \text{max: } V_{DD} - \sqrt{\frac{2I_D}{K_n \left(\frac{W}{L}\right)_7}} - \sqrt{\frac{2I_D}{K_n \left(\frac{W}{L}\right)_5}} \\ \text{min: } V_{SS} + \sqrt{\frac{2I_D}{K_n \left(\frac{W}{L}\right)_4}} + \sqrt{\frac{2I_D}{K_n \left(\frac{W}{L}\right)_2}} + \sqrt{\frac{2I_D}{K_n \left(\frac{W}{L}\right)_9}} \end{array}$$



M7 noise

$$i_{o7}^2 = 4kT g_{m7}$$

M5 noise

$$i_{o5}^2 = \frac{V_{n2}^2}{\left(\frac{1}{g_{m5}} + r_{ds1}\right)^2}$$

$$= \frac{4kT}{g_{m5}} \times \frac{1}{\left(\frac{1}{g_{m5}} + r_{ds1}\right)^2}$$

M4 noise

$$i_{n4}^2 = \frac{V_{n1}^2}{\left(\frac{1}{g_{m4}} + r_{ds2}\right)^2}$$

$$i_{n4}^2 = \frac{4kT}{g_{m4}} \times \frac{1}{\left(\frac{1}{g_{m4}} + r_{ds2}\right)^2}$$

$$i_{o \text{ total}}^2 \text{ (M2 M4)} = 4kT g_{m2} + \frac{4kT}{g_{m4}} \times \frac{1}{\left(\frac{1}{g_{m4}} + r_{ds2}\right)^2}$$

$$= 4kT \left(g_{m2} + \frac{1}{g_{m4} \left(\frac{1}{g_{m4}} + r_{ds2}\right)^2} \right)$$

$$\approx 4kT g_{m2}$$

$$i_{o \text{ total}}^2 \text{ (M1 M5)} \approx 4kT g_{m7}$$

$$V_{in \text{ noise}}^2 = \frac{i_{o \text{ total}}^2}{G_m^2} = \frac{4kT (g_{m7} + g_{m2})}{g_m^2}$$

$$V_{in \text{ ref}} = \frac{K}{F_{WL} C_{ox}} + \frac{4kT (g_{m7} + g_{m2})}{g_m^2}$$