

# **ECEN 607: Advanced Analog Circuit Tech**

## **Lab 4: Op Amp Design - I**

### **Pre-lab or Lab Report**

**Name: FirstName LastName**

**UIN: \*\*\*\*\*Last Four Digits**

## Objectives




- To be able to identify the dominant noise sources.
- To study and design a single-ended telescopic op amp.


## Recommendation:

Start building common testbench setups for finding op amp parameters such as DC Gain, unity gain frequency, slew rate etc. This can be re-used for different op-amps that you will be designing in this course and later, hence saving a lot of time.

## Prelab

- In this prelab, 5.5 V NFETs and PFETs will be used.
- Do not forget to show a detailed design procedure for each design.
- The following op amp must be tested in unity feedback configuration.

Design the telescopic amplifier with  shown in Fig. 2-2. Identify the  and find the  due to the dominant noise sources. Show the hand-calculations for the input referred noise and report the estimated value.

The specifications are set in Table 2-2. Also, add the  that generates  $V_{b1}$  and  $V_{b2}$ , i.e. modify the circuit such that it presents just one current source ( $I_{bias}$ ) and two voltage sources ( $V_{DD}$  and  $V_{SS}$ ).

 


Figure 2-2: Telescopic single stage amplifier

Table 2-2: Design specifications

$V_{DD}-V_{SS}$	5.5 V
$A_{v0}$	> 70 dB
GBW	> 2 MHz
PM	> 45°
Output Swing @ gain>40dB	> 0.8 V
$C_L$	2 pF
$R_L$	100k $\Omega$
Power Dissipated	< 300 $\mu$ W
Input referred noise (10 Hz – 2 MHz)	<30 $\mu$ Vrms

## Lab Report

### Design:

1. Simulate the circuit from the prelab and adjust the transistor sizes accordingly until all specifications are met. Provide necessary plots such that you clearly show the specs are met. The output swing specification should be tested with a transient simulation.
2. Run a statistical simulation (Monte Carlos) and provide the worst-case DC Gain, GBW, Phase Margin and input referred noise. You do not have to adjust the design if the specs are not met. Comment the results.
3. Configure a unity-gain buffer and apply a differential pulse of 1 KHz, 0.4 Vpp. Show the screen shots and provide comments on the step response; 30% and 1% settling time? Ringing? Comment on the results.
4. Provide a comparison table of hand-calculated vs. final transistor sizes including the required specs vs. simulated specs.
5. Comment on your learning from this lab.